

# **PROJECT REPORT**

## **REAL-TIME CLOCK (RTC) USING VERILOG HDL**

**Submitted by:**

**SHEFIN MUHAMMED M S**

**Under the Guidance of:**

**MR.MONISH & MS.VIMALA**

**SION SEMICONDUCTOR**

**October 2025**

---

# Contents

<b>1</b>	<b>Aim</b>	<b>2</b>
<b>2</b>	<b>Objectives</b>	<b>2</b>
<b>3</b>	<b>Tools Used</b>	<b>2</b>
<b>4</b>	<b>Methodology</b>	<b>2</b>
<b>5</b>	<b>Verilog Code and TestBench</b>	<b>3</b>
5.1	Verilog Code . . . . .	3
5.2	Testbench code . . . . .	5
<b>6</b>	<b>Results</b>	<b>7</b>
6.1	Simulated Result . . . . .	7
6.2	Waveform . . . . .	8
6.3	Elaborated Design . . . . .	8
<b>7</b>	<b>Conclusion</b>	<b>8</b>

---

## 1. Aim

The aim of this project is to design and implement a **Real-Time Clock (RTC)** using Verilog HDL that can display the current time in hours, minutes, and seconds in Seven Segmented Display in format with proper rollover logic in a 24-hour format.

## 2. Objectives

- To design an RTC circuit using Verilog HDL.
- To implement counters for seconds, minutes, and hours.
- To provide automatic rollover after 23:59:59 hour.
- To display using Seven Segmented Display
- To verify the design functionality using ModelSim simulation.
- To synthesize and implement the design using Xilinx Vivado.

## 3. Tools Used

- **Software Tools:**
  - ModelSim – for simulation and waveform verification.
  - Xilinx Vivado – for synthesis and RTL implementation.

## 4. Methodology

1. The RTC is designed using Verilog HDL with three counters for hours, minutes, and seconds.
2. Each counter increments based on the clock signal and rolls over when it reaches its limit 60 for seconds and 60 for minutes, 24 for hours.
3. Display using Seven Segmented Display
4. The design includes control logic for resetting and updating the clock.
5. Simulation is performed in ModelSim to verify correct time incrementation and rollover behavior.

- 
6. The synthesized design is analyzed in Xilinx Vivado using RTL and Technology Schematic views.

## 5. Verilog Code and TestBench

### 5.1. Verilog Code

```
1 module RTC_counter #(parameter N = 9)(input clk,rst,clear,en,  
   output reg [3:0] count,output next);  
2  
3   always@(posedge clk)begin  
4     if(rst|clear)  
5       count<=0;  
6     else if(en)begin  
7       if(N==count)  
8         count<=0;  
9     else  
10      count<=count+1;  
11    end  
12  end  
13  assign next=(N==count)&&en;  
14 endmodule  
15  
16 module RTC(input clk,rst,output [3:0] hrm,hrl,minm,minl,secm,secl  
   ,output [6:0] sec_l,sec_m,min_m,min_l,hr_m,hr_l);  
17  
18 wire next_secl,next_secm,next_minl,next_minm,next_hrl,next_hrm,  
   reset_clk;  
19 wire clear_rst=(hrm==2&&hrl==3 && minm==5&&minl==9 && secm==5  
   && secl ==9); //CHECKING THE CONDITION FOR RESET THE CLK  
20  
21 //seconds  
22 RTC_counter #(9) sec_lsb (.clk(clk),.rst(rst),.clear(clear_rst)  
   ,.en(1'b1),.count(secl),.next(next_secl));  
23  
24 RTC_counter #(5) sec_msb (.clk(clk),.rst(rst),.clear(clear_rst)  
   ,.en(next_secl),.count(secm),.next(next_secm));  
25  
26 //min
```

```

27   RTC_counter #(9) min_lsb (.clk(clk),.rst(rst),.clear(clear_rst)
    ,.en(next_secm),.count(minl),.next(next_minl));
28
29   RTC_counter #(5) min_msb (.clk(clk),.rst(rst),.clear(clear_rst)
    ,.en(next_minl),.count(minm),.next(next_minm));
30
31   //hours
32
33   RTC_counter #(9) hr_lsb (.clk(clk),.rst(rst),.clear(clear_rst)
    ,.en(next_minm),.count(hrl),.next(next_hrl));
34
35   RTC_counter #(2) hr_msb (.clk(clk),.rst(rst),.clear(clear_rst)
    ,.en(next_hrl),.count(hrm),.next(next_hrm));
36
37   //MODULE INSTANTIATION FOR DISPLAYING THE OUTPUT USING 7
    SEGMENTED DISPLAY
38   seven_segmented_dis s1(.bcd(sec1),.sev_dis(sec_1));
39   seven_segmented_dis sm(.bcd(secm),.sev_dis(sec_m));
40   seven_segmented_dis mm(.bcd(minm),.sev_dis(min_m));
41   seven_segmented_dis ml(.bcd(minl),.sev_dis(min_l));
42   seven_segmented_dis hm(.bcd(hrm),.sev_dis(hr_m));
43   seven_segmented_dis hl(.bcd(hrl),.sev_dis(hr_l));
44
45
46   endmodule
47
48
49   //CODE FOR SEVEN SEGMENTED DISPLAY
50   module seven_segmented_dis(input [3:0]bcd,output reg [6:0]sev_dis
    );
51   always@(*)begin
52       case(bcd)
53           4'd0: sev_dis = 7'b1111110;
54           4'd1: sev_dis = 7'b0110000;
55           4'd2: sev_dis = 7'b1101101;
56           4'd3: sev_dis = 7'b1111001;
57           4'd4: sev_dis = 7'b0110011;
58           4'd5: sev_dis = 7'b1011011;
59           4'd6: sev_dis = 7'b1011111;

```

```

60         4'd7: sev_dis = 7'b1110000;
61         4'd8: sev_dis = 7'b1111111;
62         4'd9: sev_dis = 7'b1111011;
63         default: sev_dis = 7'b0000000;
64     endcase
65
66 end
67 endmodule

```

## 5.2. Testbench code

```

1  //TESTBENCH CODE FOR RTC
2  module RTC_counter_tb;
3      reg clk,rst;
4      wire [3:0] hrm,hr1,minm,minl,secm,secl;
5      wire [6:0] sec_l,sec_m,min_m,min_l,hr_m,hr_l;
6
7      RTC dut(.clk(clk),.rst(rst),.hrm(hrm),
8          .hr1(hr1),
9          .minm(minm),
10         .minl(minl),
11         .secm(secm),
12         .secl(secl),
13         .sec_l(sec_l),
14         .sec_m(sec_m),
15         .min_m(min_m),
16         .min_l(min_l),
17         .hr_m(hr_m),
18         .hr_l(hr_l)
19         );
20
21     initial clk=0;
22     always#5 clk= ~clk;
23
24     initial begin
25         rst=1;#10
26         rst=0;
27
28         #2000000;

```

```

29
30     //rst=1;#10;
31     //rst=0;
32     //100000;
33
34     $stop;
35 end
36     // Monitor outputs
37 initial begin
38     $display("Time|HRMHRL   | MINMMINL | SECMSECL----seven
39         segmented display out");
40     $monitor("%0t | %0d%0d   %0d%0d       %0d%0d || seven display
41         out = %b | %b | %b | %b | %b | %b", $time, hrm, hrl, minm,
42         minl, secm, secl, hr_m, hr_l, min_m, min_l, sec_m, sec_l);
43 end
44 endmodule

```

## 6. Results

The Verilog-based RTC successfully counts time in hours, minutes, and seconds format. Simulation results confirm accurate rollover and timekeeping.

### 6.1. Simulated Result

```
# 199655 | 05 | 32 | 45 || seven display out = 1111110 | 1011011 | 1111001 | 1101101 | 0110011 | 1011011
# 199665 | 05 | 32 | 46 || seven display out = 1111110 | 1011011 | 1111001 | 1101101 | 0110011 | 1011111
# 199675 | 05 | 32 | 47 || seven display out = 1111110 | 1011011 | 1111001 | 1101101 | 0110011 | 1110000
# 199685 | 05 | 32 | 48 || seven display out = 1111110 | 1011011 | 1111001 | 1101101 | 0110011 | 1111111
# 199695 | 05 | 32 | 49 || seven display out = 1111110 | 1011011 | 1111001 | 1101101 | 0110011 | 1111011
# 199705 | 05 | 32 | 50 || seven display out = 1111110 | 1011011 | 1111001 | 1101101 | 1011011 | 1111110
# 199715 | 05 | 32 | 51 || seven display out = 1111110 | 1011011 | 1111001 | 1101101 | 1011011 | 0110000
# 199725 | 05 | 32 | 52 || seven display out = 1111110 | 1011011 | 1111001 | 1101101 | 1011011 | 1101101
# 199735 | 05 | 32 | 53 || seven display out = 1111110 | 1011011 | 1111001 | 1101101 | 1011011 | 1111001
# 199745 | 05 | 32 | 54 || seven display out = 1111110 | 1011011 | 1111001 | 1101101 | 1011011 | 0110011
# 199755 | 05 | 32 | 55 || seven display out = 1111110 | 1011011 | 1111001 | 1101101 | 1011011 | 1011011
# 199765 | 05 | 32 | 56 || seven display out = 1111110 | 1011011 | 1111001 | 1101101 | 1011011 | 1011111
# 199775 | 05 | 32 | 57 || seven display out = 1111110 | 1011011 | 1111001 | 1101101 | 1011011 | 1110000
# 199785 | 05 | 32 | 58 || seven display out = 1111110 | 1011011 | 1111001 | 1101101 | 1011011 | 1111111
# 199795 | 05 | 32 | 59 || seven display out = 1111110 | 1011011 | 1111001 | 1101101 | 1011011 | 1111011
# 199805 | 05 | 33 | 00 || seven display out = 1111110 | 1011011 | 1111001 | 1111001 | 1111110 | 1111110
# 199815 | 05 | 33 | 01 || seven display out = 1111110 | 1011011 | 1111001 | 1111001 | 1111110 | 0110000
# 199825 | 05 | 33 | 02 || seven display out = 1111110 | 1011011 | 1111001 | 1111001 | 1111110 | 1101101
# 199835 | 05 | 33 | 03 || seven display out = 1111110 | 1011011 | 1111001 | 1111001 | 1111110 | 1111001
# 199845 | 05 | 33 | 04 || seven display out = 1111110 | 1011011 | 1111001 | 1111001 | 1111110 | 0110011
# 199855 | 05 | 33 | 05 || seven display out = 1111110 | 1011011 | 1111001 | 1111001 | 1111110 | 1011011
# 199865 | 05 | 33 | 06 || seven display out = 1111110 | 1011011 | 1111001 | 1111001 | 1111110 | 1011111
# 199875 | 05 | 33 | 07 || seven display out = 1111110 | 1011011 | 1111001 | 1111001 | 1111110 | 1110000
# 199885 | 05 | 33 | 08 || seven display out = 1111110 | 1011011 | 1111001 | 1111001 | 1111110 | 1111111
# 199895 | 05 | 33 | 09 || seven display out = 1111110 | 1011011 | 1111001 | 1111001 | 1111110 | 1111011
# 199905 | 05 | 33 | 10 || seven display out = 1111110 | 1011011 | 1111001 | 1111001 | 0110000 | 1111110
# 199915 | 05 | 33 | 11 || seven display out = 1111110 | 1011011 | 1111001 | 1111001 | 0110000 | 0110000
# 199925 | 05 | 33 | 12 || seven display out = 1111110 | 1011011 | 1111001 | 1111001 | 0110000 | 1101101
# 199935 | 05 | 33 | 13 || seven display out = 1111110 | 1011011 | 1111001 | 1111001 | 0110000 | 1111001
# 199945 | 05 | 33 | 14 || seven display out = 1111110 | 1011011 | 1111001 | 1111001 | 0110000 | 0110011
# 199955 | 05 | 33 | 15 || seven display out = 1111110 | 1011011 | 1111001 | 1111001 | 0110000 | 1011011
# 199965 | 05 | 33 | 16 || seven display out = 1111110 | 1011011 | 1111001 | 1111001 | 0110000 | 1011111
# 199975 | 05 | 33 | 17 || seven display out = 1111110 | 1011011 | 1111001 | 1111001 | 0110000 | 1110000
# 199985 | 05 | 33 | 18 || seven display out = 1111110 | 1011011 | 1111001 | 1111001 | 0110000 | 1111111
# 199995 | 05 | 33 | 19 || seven display out = 1111110 | 1011011 | 1111001 | 1111001 | 0110000 | 1111011
# 200005 | 05 | 33 | 20 || seven display out = 1111110 | 1011011 | 1111001 | 1111001 | 1101101 | 1111110
```

Figure 1: Simulated Result

```
# 863905 | 23 | 59 | 50 || seven display out = 1101101 | 1111001 | 1011011 | 1111011 | 1011011 | 1111110
# 863915 | 23 | 59 | 51 || seven display out = 1101101 | 1111001 | 1011011 | 1111011 | 1011011 | 0110000
# 863925 | 23 | 59 | 52 || seven display out = 1101101 | 1111001 | 1011011 | 1111011 | 1011011 | 1101101
# 863935 | 23 | 59 | 53 || seven display out = 1101101 | 1111001 | 1011011 | 1111011 | 1011011 | 1111001
# 863945 | 23 | 59 | 54 || seven display out = 1101101 | 1111001 | 1011011 | 1111011 | 1011011 | 0110011
# 863955 | 23 | 59 | 55 || seven display out = 1101101 | 1111001 | 1011011 | 1111011 | 1011011 | 1011011
# 863965 | 23 | 59 | 56 || seven display out = 1101101 | 1111001 | 1011011 | 1111011 | 1011011 | 1011111
# 863975 | 23 | 59 | 57 || seven display out = 1101101 | 1111001 | 1011011 | 1111011 | 1011011 | 1110000
# 863985 | 23 | 59 | 58 || seven display out = 1101101 | 1111001 | 1011011 | 1111011 | 1011011 | 1111111
# 863995 | 23 | 59 | 59 || seven display out = 1101101 | 1111001 | 1011011 | 1111011 | 1011011 | 1111011
# 864005 | 00 | 00 | 00 || seven display out = 1111110 | 1111110 | 1111110 | 1111110 | 1111110 | 1111110
# 864015 | 00 | 00 | 01 || seven display out = 1111110 | 1111110 | 1111110 | 1111110 | 1111110 | 0110000
# 864025 | 00 | 00 | 02 || seven display out = 1111110 | 1111110 | 1111110 | 1111110 | 1111110 | 1101101
# 864035 | 00 | 00 | 03 || seven display out = 1111110 | 1111110 | 1111110 | 1111110 | 1111110 | 1111001
# 864045 | 00 | 00 | 04 || seven display out = 1111110 | 1111110 | 1111110 | 1111110 | 1111110 | 0110011
# 864055 | 00 | 00 | 05 || seven display out = 1111110 | 1111110 | 1111110 | 1111110 | 1111110 | 1011011
# 864065 | 00 | 00 | 06 || seven display out = 1111110 | 1111110 | 1111110 | 1111110 | 1111110 | 1011111
# 864075 | 00 | 00 | 07 || seven display out = 1111110 | 1111110 | 1111110 | 1111110 | 1111110 | 1110000
# 864085 | 00 | 00 | 08 || seven display out = 1111110 | 1111110 | 1111110 | 1111110 | 1111110 | 1111111
```

Figure 2: Roll Over after 23:59:59



## 6.2. Waveform

 


Figure 3: Waveform

## 6.3. Elaborated Design

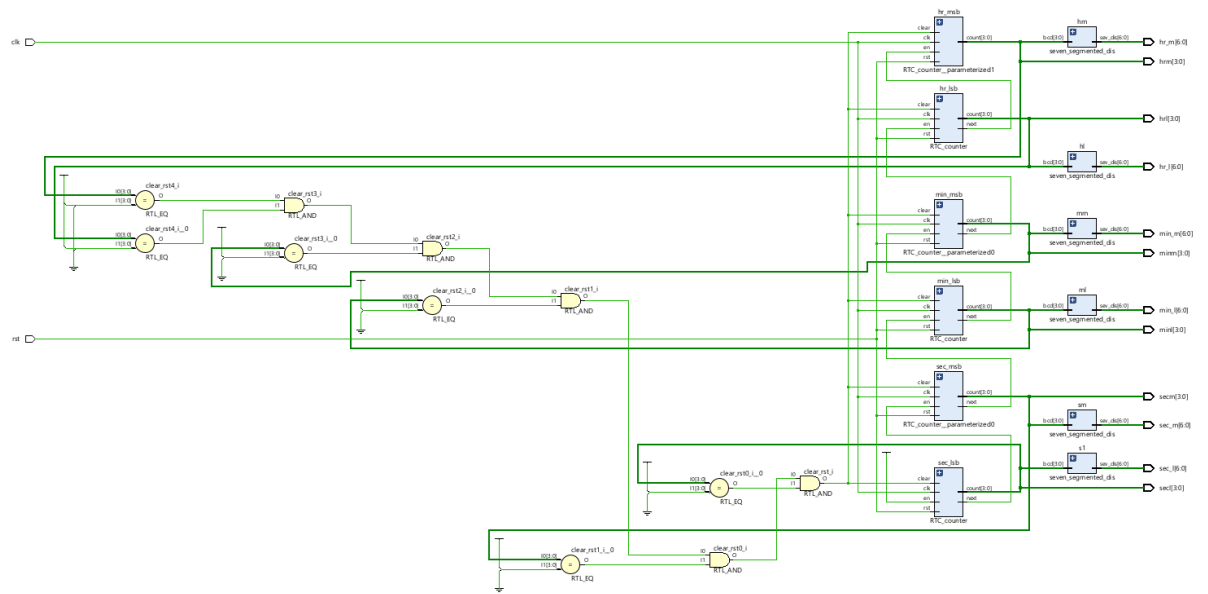


Figure 4: Elaborated Design using Vivado

## 7. Conclusion

The project demonstrates the design and verification of a Real-Time Clock using Verilog HDL. The system efficiently counts and displays real-time values, proving useful for various timing-based digital systems.